

Technology Independent Logic Optimization

Prof. Kurt Keutzer
EECS
University of California
Berkeley, CA

Thanks to R. Rudell, S. Malik

1


Outline

- Motivation for Multilevel
- Overview of Techniques
- Details on multilevel techniques

2-Level => Programmable Logic Arrays (PLAs)

We can represent any Boolean function in a 2-level/SOP form


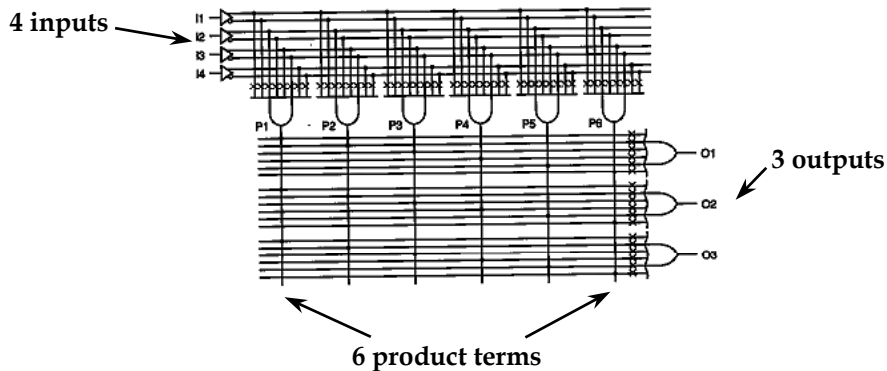
Any such representation can be implemented in a PLA




Kurt Keutzer

3

Early "Synthesis" Flow

  

$$F1 = B + D + AC + AC$$

 

Kurt Keutzer

4

Why Multilevel Combinational Circuits?

There are many functions that are too “expensive” to implement in two-level form

Try 16-bit adder \Rightarrow 32 input lines and 2^{16} product terms!

2-level: control logic design

multi-level: datapath logic or random logic

Two-Level versus Multilevel

Even simple functions expressed in 2-Level:

$$f_1 = AB + AC + AD$$

$$f_2 = \bar{A}B + \bar{A}C + \bar{A}E$$

6 product terms which cannot be shared.

24 transistors in static CMOS

May be more efficient in multi-level:

Note that $B + C$ is a common term in f_1 and f_2

$$K = B + C$$

3 Levels

20 transistors in static CMOS
not counting inverters


$$f_1 = AK + AD$$

$$f_2 = \bar{A}K + \bar{A}E$$


Outline

- Motivation for Multilevel
- Overview of Techniques
- Details on multilevel techniques

RTL Design Flow

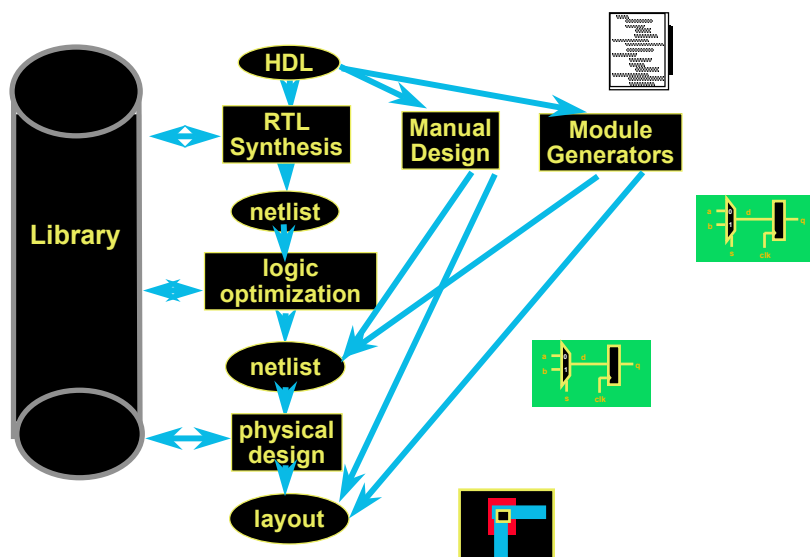


Logic Optimization

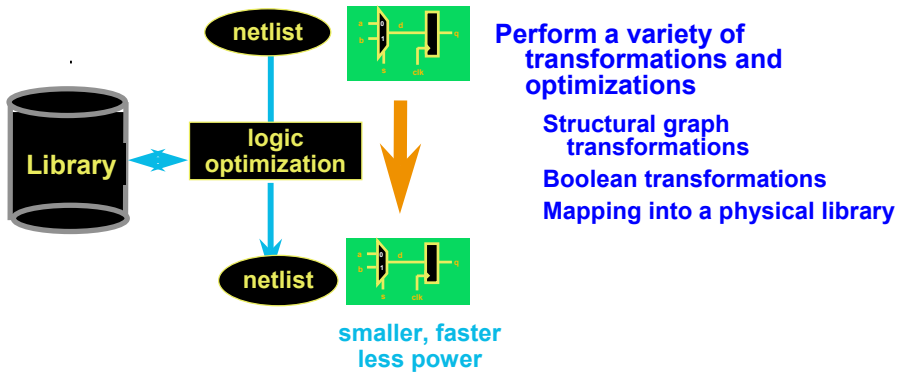

Kurt Keutzer

9

Reduce to Combinational Optimization

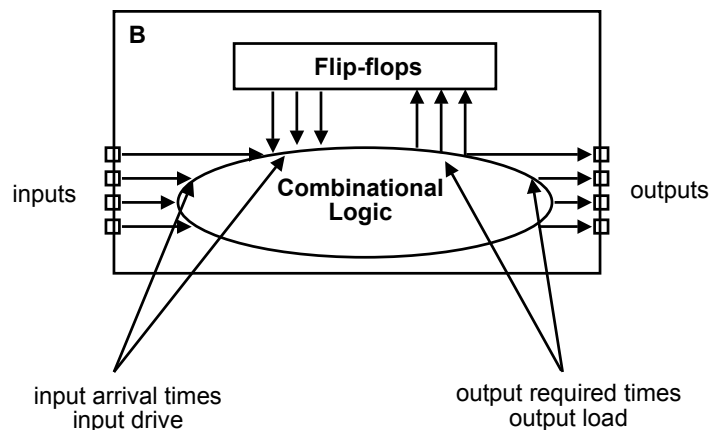

Kurt Keutzer

10

Representation: Boolean Network

A *Boolean network* is designated $\eta = (\underline{y}, \underline{H})$ where:

$\underline{y} = (y_1, K, y_{n+m+r})$ is a vector of variables

$\underline{H} = (H_1, K, H_{n+m+r})$ is a vector of functions

y_1, K, y_n are the primary input variables

y_{n+1}, K, y_{n+r} are the intermediate variables

y_{n+r+1}, K, y_{n+m+r} are the primary output variables


$y_i = H_i(y_1, K, y_{n+m+r})$

A Boolean network has an associated graph

which shows the function dependencies;

i.e., the edge (i, j) is present if $y_i \in \text{sup}(H_j)$.
 
$$\begin{aligned} y_5 &= H_5 = \bar{y}_1 y_2 \\ y_6 &= H_6 = y_3 y_4 \\ y_7 &= H_7 = y_1 \bar{y}_6 + y_2 \\ y_8 &= H_8 = y_5 + y_6 \\ y_9 &= H_9 = y_7 \\ y_{10} &= H_{10} = y_8 \end{aligned}$$



Kurt Keutzer

11

Combinational Logic Optimization

Input:

Initial Boolean network

Timing characterization for the module

- input arrival times and drive factors

- output loading factors

Optimization goals

- output required times

Target library description

Output:

Minimum-area net-list of library gates which meets timing constraints

A very difficult optimization problem !

Kurt Keutzer

12

Modern Approach to Logic Optimization

Divide logic optimization into two subproblems:

- Technology-independent optimization
 - determine overall logic structure
 - estimate costs (mostly) independent of technology
 - simplified cost modeling
- Technology-dependent **optimization** (technology mapping)
 - binding onto the gates in the library
 - detailed technology-specific cost model

Orchestration of various optimization/transformation techniques for each subproblem

Formats

Boolean Network, Boolean equations


Generic library – technology independent

- Has standard functions – ND2, ND4, AOI22, pos-edge-FF
- only an estimate of timing

Actual technology library

- Represents logic functions and their physical characteristics of a library cells offered by a particular silicon vendor – e.g. TSMC
- E.g. captured in .lib file
- Contains complete logical, timing information

Logic Optimization

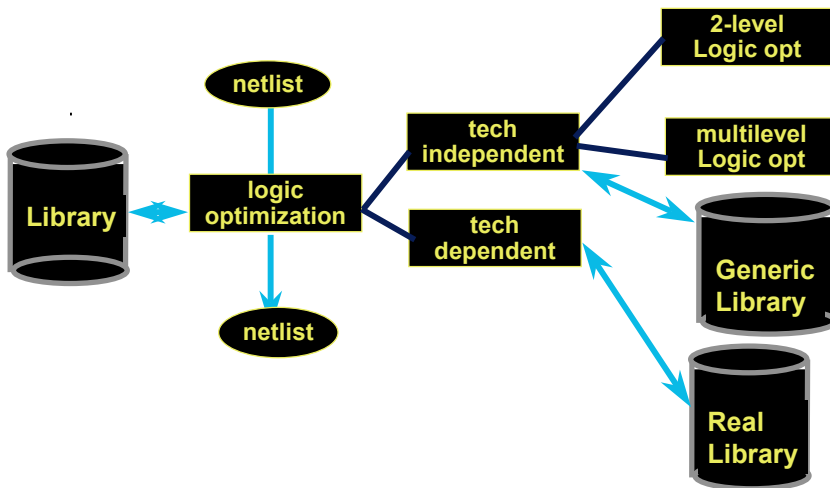

Kurt Keutzer

15

Tech.-Independent Optimization

Involves:

Minimizing two-level logic functions.

Finding common subexpressions.

Substituting one expression into another.

Factoring single functions.

Factored versus Disjunctive forms

$$f = ac + ad + bc + bd + a\bar{e}$$

sum-of-products or disjunctive form

$$f = (a + b)(c + d) + a\bar{e}$$

factored form

multi-level or complex gate

Kurt Keutzer

16

Decomposition

G is a *Boolean divisor* of F if $F = G \cdot H + R$ for functions $H \neq 0, R \neq 0$

Searching for divisors which are common to many functions in the network

Decomposition:

identify divisors which are common to several functions

introduce common divisor as a new node

re-express existing nodes using the new divisor

Technology-independent measure of cost to measure *goodness*

area cost: total number of literals

delay cost: levels of logic on the critical path

Division

- If $h \neq 0$, and h can be obtained using algebraic division, then g is an **algebraic divisor** of f . Otherwise, g is a **Boolean divisor** of f .
- Example:
$$\begin{aligned}f &= ad + ae + bcd + j \\g_1 &= a + bc \\g_2 &= a + b\end{aligned}$$
- Algebraic division $f//a = d + e, f//(bc) = d$
- Also,
 $f//a = d$ or $f//a = e$, i.e. algebraic division is not unique) $h_1 = f//g_1 = d, r_1 = ae + j$
- Boolean division: $h_2 = f \div g_2 = (a + c)d, r_2 = ae + j$.
i.e. $f = (a+b)(a+c)d + ae + j$

Strong (or Boolean) Division

Given a function f to be strong divided by g

Add an extra input to f corresponding to g ,
namely G and obtain function h as follows

$$h_{DC} = G\bar{g} + \bar{G}g$$

$$h_{ON} = f_{ON} - h_{DC}$$

$$h_{OFF} = \overline{f_{ON} + h_{DC}}$$

Minimize h using two-level minimizer

Algebraic vs. Boolean Methods

Algebraic techniques view equations as
polynomials and attempt to factor equations or
“divide” them

Do not exploit Boolean identities e.g., $a\bar{a} = 0$

In algebraic substitution (or division) if a function
 $f = f(a, b, c)$ is divided by $g = g(a, b)$, a and b
will not appear in f/g

Algebraic division: $O(n \log n)$ time

Boolean division: unmanageable number of
divisors

Comparison of factorization

$$f = a\bar{b} + a\bar{c} + b\bar{a} + b\bar{c} + c\bar{a} + c\bar{b}$$

Algebraic factorization procedures

$$f = a(\bar{b} + \bar{c}) + \bar{a}(b + c) + b\bar{c} + c\bar{b}$$

Boolean factorization produces

$$f = (a + b + c)(\bar{a} + \bar{b} + \bar{c})$$

Comparison

Substitution is the factoring of one node in the Boolean Network (e.g. l) by another (e.g. r)

Algebraic substitution of l into r fails

Boolean substitution yields results

$$l = (b\bar{f} + \bar{b}f)(a + e) + \bar{a}\bar{e}(\bar{b}f + bf)$$

$$r = (b\bar{f} + \bar{b}f)(\bar{a} + \bar{e}) + ae(\bar{b}f + bf)$$

After resub:

$$r = a(\bar{e}\bar{l} + el) + \bar{a}(\bar{e}l + e\bar{l})$$

$$l = a(er + \bar{e}\bar{r}) + \bar{a}(\bar{e}r + e\bar{r})$$

Algebraic Decomposition

Algebraic approximation (informal definition)

- simplify Boolean function using two-level minimization
- treat result as a polynomial; i.e.,

x_i and \bar{x}_i are different variables
i.e., $x_i \cdot \bar{x}_i \neq 0$ and $x_i \cdot x_i \neq x_i$

- identify common divisors as algebraic divisors of the polynomials

Algebraic Decomposition

Algebraic approximation (informal definition)

- simplify Boolean function using two-level minimization
- treat result as a polynomial; i.e.,

x_i and \bar{x}_i are different variables
i.e., $x_i \cdot \bar{x}_i \neq 0$ and $x_i \cdot x_i \neq x_i$

- identify common divisors as algebraic divisors of the polynomials

Motivation

- manipulating polynomials is fast (linear time algorithms)
- # algebraic divisors still exponential, but usually manageable
- loss of optimality, but experimentally shows good results
- interleave Boolean simplification procedures to improve results

Algebraic Decomposition

Algebraic approximation (informal definition)

- simplify Boolean function using two-level minimization
- treat result as a polynomial; i.e.,

x_i and \bar{x}_i are different variables
i.e., $x_i \cdot \bar{x}_i \neq 0$ and $x_i \cdot x_i \neq x_i$

- identify common divisors as algebraic divisors of the polynomials

Techniques

- single-cube algebraic divisors (common-cube decomposition)
- multiple-cube algebraic divisors (kernel decomposition)

Decomposition?

$$F = a d e + b d e + c d e + f$$

$$G = b g + c g + d g + a e f$$

$$H = a e g + b c$$

How can this logic be further simplified?

Common Cube Decomposition

$$\begin{aligned} F &= ade + bde + cde + f \\ G &= bg + cg + dg + aef \\ H &= aeg + bc \end{aligned}$$



$$\begin{aligned} F &= Xd + bde + cde + f \\ G &= bg + cg + dg + Xf \\ H &= Xg + bc \\ X &= ae \end{aligned}$$

Finds algebraic divisors which are single cubes

"Common cubes" are easy to detect

Greedy algorithm:

- enumerate all maximal common cubes
- select cube which saves the most literals
- add node to the network and re-express affected nodes
- repeat until no common cubes remain

References: [Dietmeyer-69], [Brayton-82], [Rudell-89]

Kurt Keutzer

27

Kernel Decomposition

$$\begin{aligned} F &= ade + bde + cde + f \\ G &= bg + cg + dg + aef \\ H &= aeg + bc \end{aligned}$$



$$\begin{aligned} F &= (a + b + c)de + f \\ G &= (b + c + d)g + aef \\ H &= aeg + bc \end{aligned}$$



$$\begin{aligned} F &= (a + X)de + f \\ G &= (X + d)g + aef \\ H &= aeg + bc \\ X &= b + c \end{aligned}$$

cube-free: an expression is cube-free if no literal appears in every cube

kernel: A kernel of an expression is a cube-free divisor which is not contained in any other cube-free divisor (e.g., $a + b + c$ is a kernel of F , while $b + c$ is not a kernel because it is contained in $a + b + c$)

Kernels are useful because:

- if f and g share a common multiple-cube divisor, then the intersection of some kernel from f and some kernel from g yields a common multiple-cube divisor [Brayton-82].
- practical algorithms exist to find intersections of kernels [Rudell-89].
- kernel decomposition finds solutions which are difficult to find using only common-cube decomposition

Kurt Keutzer

28

Selective Collapsing

"Collapse" nodes into their fanout to increase the size of each node

$$\begin{array}{l} f = a h + b h' + c d \\ g = b h \\ h = a c + d' \end{array}$$

collapse h

$$\begin{array}{l} f = a (a c + d') + b (a' d' + c' d') + c d \\ g = b (a c + d') \end{array}$$

simplify

$$\begin{array}{l} f = a c + a d' + a' b d' + b c' d' + c d \\ g = a b c + b d' \end{array}$$

Goals:

- remove bad initial structure
- reduce logic level depth
- expose further optimization opportunities

Summary of Typical Recipe

Selective-collapse

Simplify: Two-level minimization at Boolean network node

Structuring/Algebraic decomposition

Local Boolean optimizations

Tree-covering for gate selection

Load-buffering for fanout-tree construction

Local transformation improvement of circuit structure

Restructure and iterate if timing constraints not met

Technology Independent Optimization

Technology Mapping

Outline

- Motivation for Multilevel
- Overview of Techniques
- Details on multilevel techniques

Decomposition - details

$$F = \begin{cases} f_1 = AB + AC + AD + AE + \overline{A}\overline{B}\overline{C}\overline{D}\overline{E} \\ f_2 = \overline{A}B + \overline{A}C + \overline{A}D + \overline{A}F + \overline{A}\overline{B}\overline{C}\overline{D}F \end{cases}$$

Factor F

$$F = \begin{cases} f_1 = A(B + C + D + E) + \overline{A}\overline{B}\overline{C}\overline{D}\overline{E} \\ f_2 = \overline{A}(B + C + D + F) + \overline{A}\overline{B}\overline{C}\overline{D}F \end{cases}$$

Extract common expression

$$G = \begin{cases} g_1 = B + C + D \\ f_1 = A(g_1 + E) + \overline{A}\overline{E}\overline{g_1} \\ f_2 = \overline{A}(g_1 + F) + \overline{A}\overline{F}\overline{g_1} \end{cases}$$

Representation: Boolean Network

A Boolean network is designated $\eta = (\underline{y}, \underline{H})$ where:

$\underline{y} = (y_1, K, y_{n+m+r})$ is a vector of variables

$\underline{H} = (H_1, K, H_{n+m+r})$ is a vector of functions

y_1, K, y_n are the primary input variables


y_{n+1}, K, y_{n+r} are the intermediate variables

y_{n+r+1}, K, y_{n+m+r} are the primary output variables

$y_i = H_i(y_1, K, y_{n+m+r})$

A Boolean network has an associated graph which shows the function dependencies; i.e., the edge (i, j) is present if $y_i \in \text{sup}(H_j)$.
 
$$\begin{aligned} y_5 = H_5 &= \bar{y}_1 y_2 \\ y_6 = H_6 &= y_3 y_4 \\ y_7 = H_7 &= y_1 \bar{y}_6 + y_2 \\ y_8 = H_8 &= y_5 + y_6 \\ y_9 = H_9 &= y_7 \\ y_{10} = H_{10} &= y_8 \end{aligned}$$



Kurt Keutzer

33

Weak (or Algebraic) Division

Definition: *support* of f , denoted $\text{sup}(f) = \{ \text{set of all variables } v \text{ that occur in } f \text{ as } \bar{v} \text{ or } v \}$

Example: $f = A \bar{B} + C$

$$\text{sup}(f) = \{ A, B, C \}$$

Kurt Keutzer

34

Weak (or Algebraic) Division

Definition: *support* of f , denoted $sup(f) = \{ \text{set of all variables } v \text{ that occur in } f \text{ as } \overline{v} \text{ or } v \}$

Example: $f = A\overline{B} + C$
 $sup(f) = \{ A, B, C \}$

Definition: we say that f is orthogonal to g , $f \perp g$, if $sup(f) \cap sup(g) = \phi$

Example: $f = A + B$ $g = C + D$
 $\therefore f \perp g$ since $\{ A, B \} \cap \{ C, D \} = \phi$

Weak Division - 2

We say that g divides f weakly if there exist h, r such that $f = gh + r$ where $h \neq \phi$ and $g \perp h$

Example: $f = ab + ac + d$
 $g = b + c$
 $f = a(b + c) + d$ $h = a$ $r = d$

We say that g divides f evenly if $r = \phi$

The *quotient* f/g is the largest h such that $f = gh + r$ i.e., $f = (f/g)g + r$

Computing f/g

Given $f = \{c_i\}$, $g = \{a_i\}$ i.e., lists of sets of cubes

$$h_i = \{b_j \mid a_i b_j \in f\} \forall i$$

i.e., all the multipliers of the cube a_i in g that produce elements of f are in h_i

$$\text{Theorem: } f/g = \bigcap_{i=1}^{|g|} h_i = h_1 \cap h_2 \dots h_{|g|}$$

Weak Division Example

$$f = abc + abde + abh + bcd$$

$$g = c + de + h$$

Theorem says $f/g = f/c \cap f/de \cap f/h$

$$f/c = ab + bd$$

$$f/de = ab$$

$$f/h = ab$$

$$f/g = (ab + bd) \cap ab \cap ab = ab$$

$$f = ab(c + de + h) + bcd$$

Time complexity: $O(|f| |g|)$. $|f|$ the number of cubes in f

Types of Algebraic Divisors

Define divisors of f as the set

$$D(f) = \{ g \mid f/g \neq \phi \}$$

Define primary divisors of f as

$$P(f) = \{ f/c \mid c \text{ is a cube} \}$$

Example: $f = abc + abde$
 $f/a = bc + bde$ is a primary divisor

Every divisor of f is contained in a primary divisor. If g divides f , then $g \subseteq p \in P(f)$

g is termed “cube-free” if the only cube dividing g evenly is 1.

Kernels and Divisors

Define the kernels of f as

$$K(f) = \{ k \mid k \in P(f), k \text{ is cube-free} \}$$

Example: $f = abc + abde$

$f/a = bc + bde$ is a primary divisor
but is not cube-free since b is a factor
 $f/a = b(c + de)$

$f/ab = c + de$ is a kernel

ab is the co-kernel

The co-kernel of a kernel is not unique.

Examples

Consider

$$f = acd + bcd + ae + be$$

DIVISOR TYPE?

$$f/a = cd + e$$

$$f/c = ad + bd$$

$$f/cd = a + b$$

$$f/e = a + b$$

Common Divisors and Kernels

Goal of multi-level logic optimizer is to find common divisors of two (or more) functions f and g

Theorem: f and g have a non-trivial common divisor d ($d \neq \text{cube}$) if and only if there exist kernels

$k_f \in K(f)$, $k_g \in K(g)$ such that
 $k_f \cap k_g$ is non-trivial, i.e., not a cube

\therefore can use kernels of f and g to locate common divisors

Algorithm to find All Kernels

```

Kernels(f)
  Find  $c_f$  so  $f/c_f$  is cube-free ;
   $K = \text{Kernel1}(0, f/c_f)$  ;
  if (f is cube-free)
    return( $f \cup K$ ) ;
  return( $K$ ) ;

Kernel1(j, g) {
   $R = g$  ;
  /* n = number of literals */
  for ( $i=j+1$ ;  $i \leq n$ ;  $i=i+1$ ) {
    if ( $l_i$  in one or no terms) continue ;
     $c_e = \text{Max. literal cube evenly dividing } (g/l_i) l_i$  ;
    if ( $l_k$  not in  $c_e$ , for all  $k \leq i$ )
       $R = R \cup \text{Kernel1}(i, (g/l_i)/c_e)$ 
  }
  return( $R$ ) ;      {Presume ordering on literals}

```

Kurt Keutzer

43

Kerneling Example

$$f = abcd + abce + adgh + aegh + abde + acdeg + beh$$

co-kernel

kernel

1	$a(bc + gh)(d + e) + ade(b + cg) + beh$
a	$(bc + gh)(d + e) + de(b + cg)$
ab	$c(d + e) + de$
abc	$d + e$
abd	$c + e$
ac	$b(d + e) + deg$
acd	$b + eg$
ace	$b + dg$
ad	$b(c + e) + g(ce + h)$
ade	$b + cg$
adg	$ce + h$

⋮

Kurt Keutzer

44

Orchestration of Optimization Techniques

Technology-independent:

- two-level minimization
- selective collapsing
- algebraic decomposition
- restructuring for timing
- redundancy removal
- transduction
- global-flow

Technology-dependent:

- tree covering
- load buffering
- rule-based mapping
- signature analysis
- inverter phase assignment
- discrete sizing

Logic optimization - summary

Current formulation of logic synthesis and optimization is the most common techniques for designing integrated circuits today

Has been the most successful design paradigm 1989 - present

Almost all digital circuits are touched by logic synthesis

- Microprocessors (control portions/random glue logic ~ 20%)
- Application specific standard parts (ASSPs)- 20 - 90%
- Application specific integrated circuits (ASICs) - 40 - 100%

Real logic optimization systems orchestrate optimizations

- Technology independent
- Technology dependent
- Application specific (e.g. datapath oriented)

Computing f/g

Given $f = \{c_i\}$, $g = \{a_i\}$

- 1) Encode cubes $a_i \in g$ with unique integer codes, by assigning a unique bit position for every literal in $\text{sup}(g)$

e.g., $g = ab + e$
110 001

- 2) Encode cubes $c_j \in f$ similarly

e.g., $f = abc + abd + de$
110 110 001

- 3) Sort $\{a_i, c_j\}$ by their codes

e.g., $\overleftarrow{ab}, abc, abd, \overrightarrow{e}, de$
110 001
 $h_1 = c + d$ $h_2 = d$

