

# **Manufacture Testing of Digital Circuits**

**Prof. K-T Cheng**

**UC Santa Barbara**

**Prof. Srinivas Devadas**

**MIT**

**Prof. Kurt Keutzer**

**Mukul Prasad**

**University of California**

**Berkeley, CA**

1

## **Class News**

---

**Assignment of grade range for midterm on Wednesday**

**Preliminary project report due 11/3**

**Second midterm**

- Currently scheduled for 11/8 to be turned in 11/10!**
- Reschedule 11/8 to be turned in 11/15**

2


# Design Process

**Design** : specify and enter the design intent



 **Verify:**

verify the correctness of design and implementation




**Implement:**

refine the design through all phases




3

# Design Verification

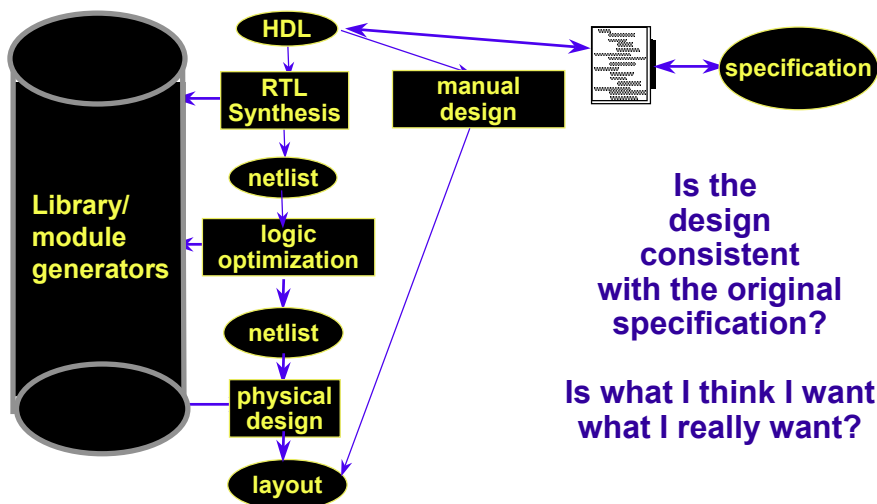


4

# Implementation Verification

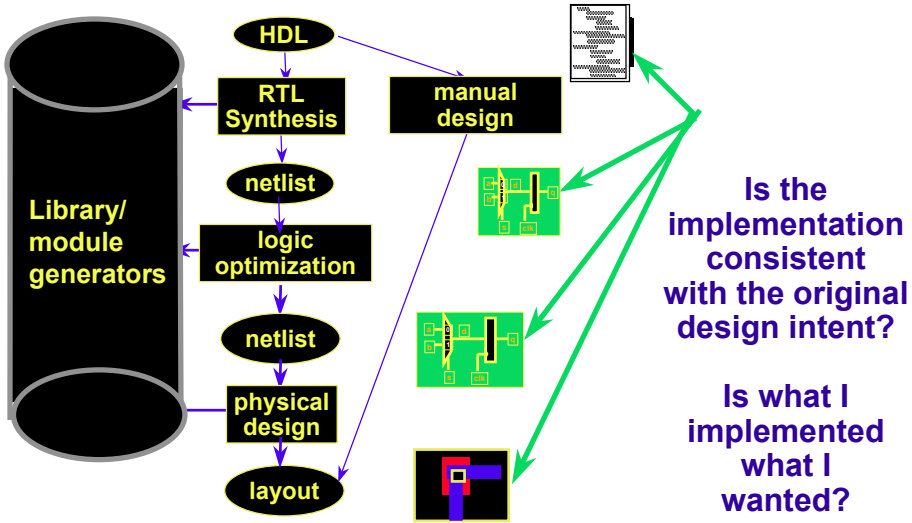

# Manufacture Verification (Test)

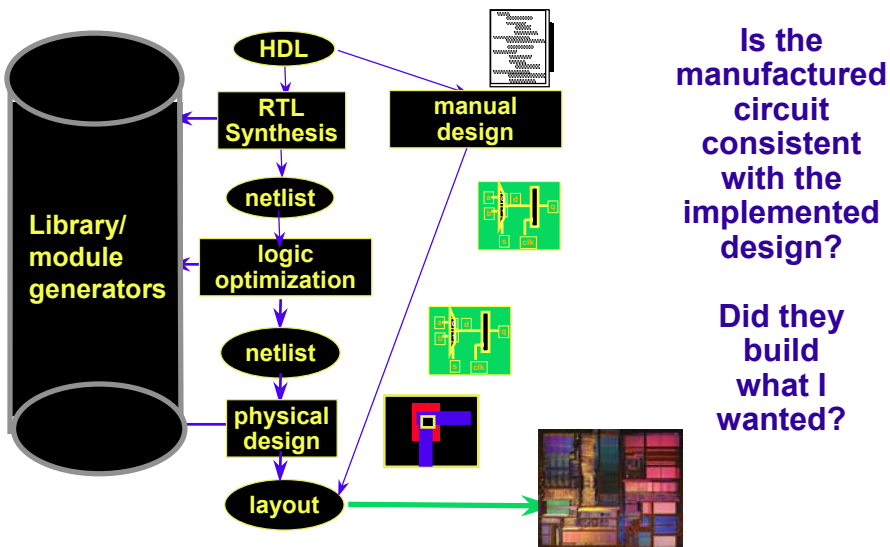


# Testing

Apply a sequence of inputs to a circuit

Observe the output response and compare the response with a precomputed or “expected” response

 Any discrepancy is said to constitute an error, the cause of which is a physical defect



7

# Defects and Fault models

Manufacturing defects can manifest in a variety of ways:

- Bridging
- Contaminants
- Shorts
- Opens
- Transistors stuck-open

These need to be reduced to models:


- Single stuck-at-1, stuck-at-0
- Multiple stuck-at-1, stuck-at-0
- Delay fault models:
  - Gate
  - Path
  - x {hazard-free, hazard-free robust}

Presently:

- single-stuck-at fault model ubiquitous
- some use of delay fault modeling

8


## Defect-related Yield Loss

 

fatal defect types (two types of short circuits, one type of open)

9

## Defect Model: Stuck-At Faults

 

Any input or internal wire in circuit can be stuck-at-1 or stuck-at-0


**Single stuck-at-fault model:** In the faulty circuit, a single line/wire is S-a-0 or S-a-1

**Multiple stuck-at fault model:** In the faulty circuit any subset of wires are S-a-0/S-a-1 (in any combination)

10
 
## Reduce to Combinational Logic Problem

add additional state to flip-flops  
(15 - 20% area overhead)



11

## Test Generation

Choose a fault model, e.g., single stuck-at fault model

Given a combinational circuit which realizes the function  $f(x_1, x_2, \dots, x_n)$ , a logical fault alters it to  $f_\infty(x_1, x_2, \dots, x_n)$

Inputs detecting  $\infty$  are  $f \oplus f_\infty (= 1)$



Interested in one vector

$$A = (a_1, a_2, \dots, a_n) \in f \oplus f_\infty$$

12
  
## Single Stuck-At Faults

A fault is assumed to occur only on a single line.




This model is used because it has been found to be statistically correlated with defect-free circuits

13
 
## Activation and Path Sensitization

In order for an input vector  $X$  to detect a fault a s-a-j,  $j = 0,1$  the input  $X$  must cause the signal  $a$  in the normal (fault-free) circuit to take the value  $\bar{j}$ .




The condition is necessary but not sufficient. Error signal must be propagated to output.

14
 
## Fault Activation

The faulty signal must be propagated along some path from its origin to an output




How to activate the fault?

15
 
## Fault Activation

The faulty signal must be propagated along some path from its origin to an output




**h s-a-1, for h to be 0, need  $x_2 = x_3 = 0$  ( $\overline{x_2} \overline{x_3}$ )**

16


 
## Fault Propagation

The error signal must be propagated along some path from its origin to an output




$h$  s-a-1, for  $h$  to be 0, need  $x_2 = x_3 = 0$  ( $\bar{x}_2 \bar{x}_3$ )

How to propagate the fault?

17
 
## Fault Propagation

The error signal must be propagated along some path from its origin to an output



$h$  s-a-1, for  $h$  to be 0, need  $x_2 = x_3 = 0$  ( $\bar{x}_2 \bar{x}_3$ )

Only one path  $G_3, G_5$

In order to propagate an error through AND gate  $G_3$ , other input  $x_1 = 1$ . To propagate through  $G_5$ , need  $G_4 = 0, x_1 + \bar{x}_4$


18

## Single Path Sensitization (SPS)

1. **Activate:** Specify inputs so as to generate the appropriate value (0 for s-a-1, 1 for s-a-0) at the site of the fault.
2. **Propagate:** Select a path from the site of the fault to an output and specify additional signal values to propagate the fault signal along this path to the output (error propagation).
3. **Justify;** Specify input values so as to produce the signal values specified in (2) (line justification).

19

## Sensitization Example - 1

 


h s-a-1

Activate?

—

20

## Sensitization Example - 2

 

h s-a-1


Activate: To generate  $h = 0$ , need  $A = B = C = 1$

Propagate?

—

21

## Sensitization Example - 2

 

h s-a-1

To generate  $h = 0$ , need  $A = B = C = 1$

Have a choice of propagating through  $G_5$  or via  $G_6$ .

Propagating through  $G_5$  requires  $G_2 = 1$


$\Rightarrow A = D = 0$  **Contradiction**

Propagating through  $G_6$  requires  $G_4 = 1 \Rightarrow C = 1, E = 0$ .

A valid test vector is  $ABC\bar{E}$

22

## Line Justification

 

$E \text{ s-a-1} \Rightarrow E = 0$


$C = D = 1$  to propagate through  $G_1$ .

To propagate through  $G_4$ , need  $G_2 = G_3 = 1$

How do we justify these values?

23

## Line Justification - 2

 

Attempt to line justify  $G_2 = G_3 = 1$

$G_3 = 1$  possible if  $A = F = 1$  or  $B = H = 1$

If  $A = C = 1$ , then  $G_2 = 0$ .

$G_3 = 1 \Rightarrow B = H = 1$


$G_2 = 1$  needs  $A = 0$  or  $F = 0$

Tests are !ABCD!EH, BCD!E!FH

24
 
# Redundancy


Existence of a fault does not change the functionality of a circuit  $\Rightarrow$  redundant fault



A test generation algorithm is deemed complete if it either finds a test for any fault or proves its redundancy, upon terminating.

25

# Completeness of SPS method ?

 

$d$  s-a-0  $\Rightarrow A = B = 1$

Propagate along  $G_3, G_6 \Rightarrow C = 1$

$G_2 = G_4 = G_5 = 1$


For  $G_4 = 1$  either  $G_1 = 0$  or  $E = 0$

If  $G_1 = 0$  fault is not activated

If  $E = 0$  (B must be 1)  $\Rightarrow G_5 = 0$  **Inconsistency**

26

## Completeness of SPS? - 2

 


Propagation along  $G_4$ ,  $G_6$  also results in inconsistencies by symmetric argument

Is there no test?

27

## Multiple Path Sensitization

 

Error propagates down two paths  $G_3$ ,  $G_6$  and  $G_4$ ,  $G_6$  to output

It's natural to work backwards (justifying) and forwards (propagating) from point of fault activation but this focuses on sensitizing a single path

Attempting to sensitize a single path will not find a test for this fault


28

## First notation: D-Algebra/ D-calculus

Need to be able to deal with multiple  
“errors” at the inputs to a gate

D represents a signal which has value 1 in  
normal circuit, and value 0 in faulty  
circuit.

$\bar{D} \equiv 0/1$

 

D,  $\bar{D}$  behave like Boolean variables

29

## Podem strategy – Goel

Podem uses a brilliant simplification to avoid the single-path  
sensitization trap - only primary inputs are assigned a value

Values are assigned to primary inputs, then propagated forward –  
need a compatibility between required value and PI value

Continue to assign PI values one at a time

- Implicate values forward
- check to see if the faulty value has propagated to an output – if so then you have a test


If at any point there is a conflict between the PIs and

- Exciting the faulty value
- Propagating the faulty value forward


backtrack – but only at the primary inputs, if you have tried all  
combinations then halt with failure to find test

30

# Podem decision procedure

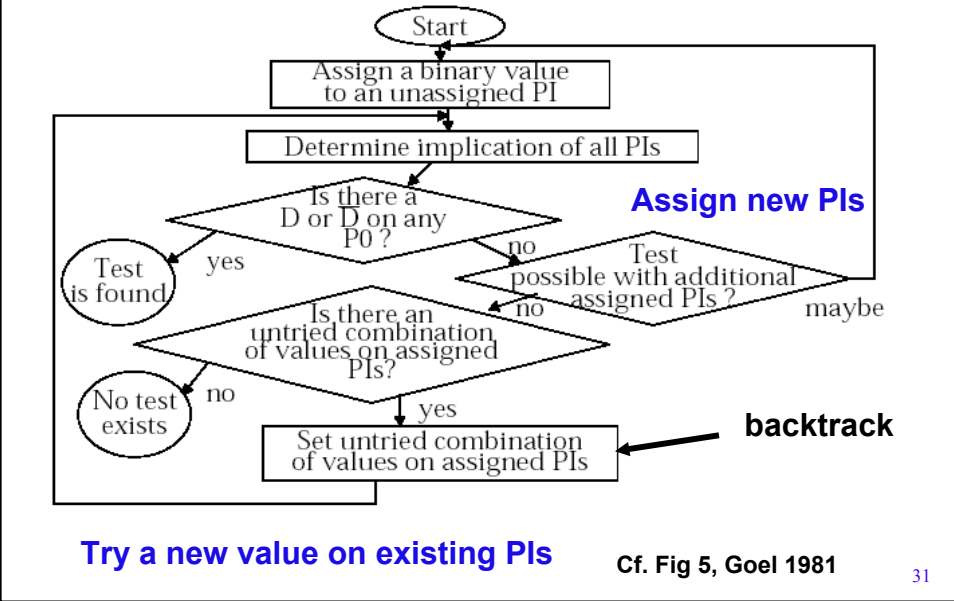

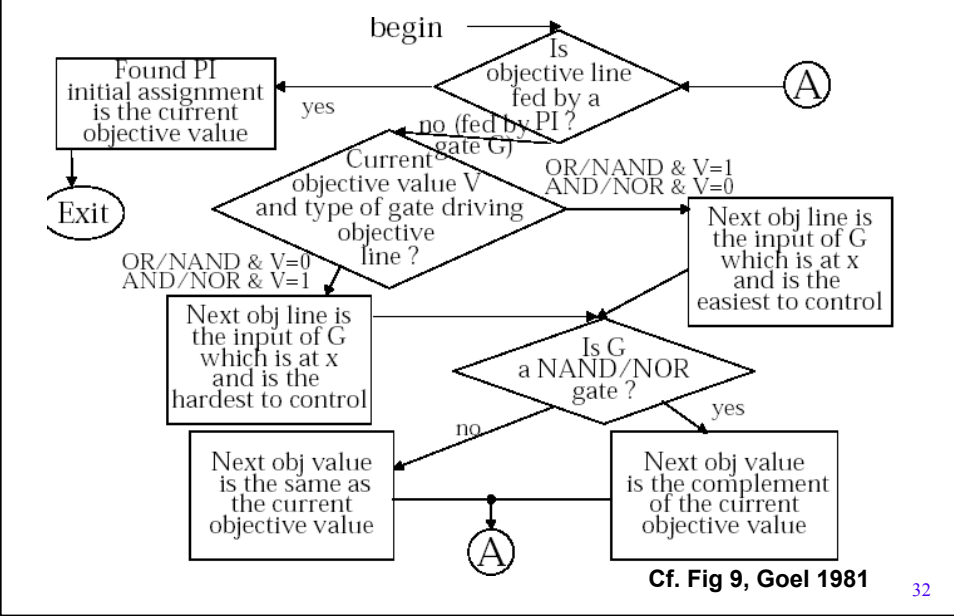
# Flowchart of Backtrace (not backtrack!)





## PODEM Example

 

Initial objective:  $(0, G_2)$

Backtrace to PIs:  $x_2 = 1$


Objective:  $(0, G_2)$

Backtrace:  $x_3 = 1$

Implication:  $G_2 = \bar{D}$

33

## Podem Example – 2a

 

D-frontier is  $\{G_5, G_6\}$


Attempt to propagate through  $G_5$

Require  $x_1 = 1$

Implication?

34

## Podem Example – 2b

 

D-frontier is  $\{G_5, G_6\}$


Attempt to propagate through  $G_5$

Require  $x_1 = 1$

Implication  $G_1 = 0, G_4 = 1, G_5 = D$

35

## Podem Example – 3a

 

Attempt to propagate  $D$  through  $G_8$ .


Objective  $(1, G_6)$

Backtrace to set  $x_4 = 0$

Implication produces  $G_3 = 1, G_7 = 0, G_8 = 1$   
failed in propagating error

36

## Podem Example – 3b

 


Attempt to propagate  $D$  through  $G_6$ .

Objective (1,  $G_6$ )

Backtrace

37

## Podem Example - 4

 

BACKTRACK to most recent assignment  $x_4$

Try alternative value  $x_4 = 1$

Implication results in  $G_3 = 0, G_6 = D, G_8 = D$

Generated test 1111

38

## Status on Podem

---

Podem approach very successful

At the core of most ATPG systems today

Spawned many additional innovations

- FAN – Fujiwara – sophisticated backtrace
- Socrates – Schulz – learning

But if we had it all to do over ...

39

## Another approach to ATPG

---

The ATPG problem


The CIRCUIT-SAT problem

The Boolean Satisfiability (SAT) problem



40


## The ATPG problem

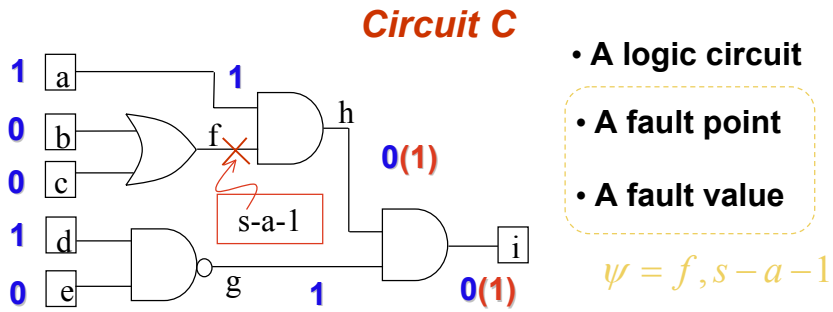

*Does there exist a value assignment to the primary inputs which distinguishes the faulted and correct circuits ?*

41

## The CIRCUIT-SAT problem

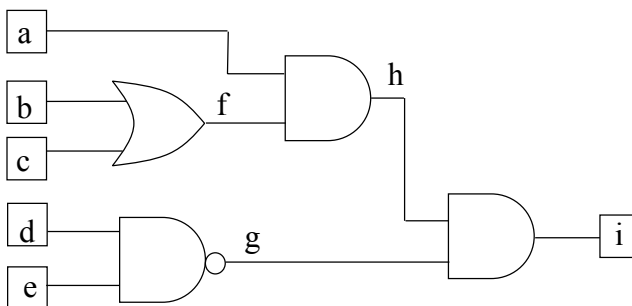


*Does there exist a value assignment to the primary inputs which causes at least one primary output to assume logic value '1' ?*

42
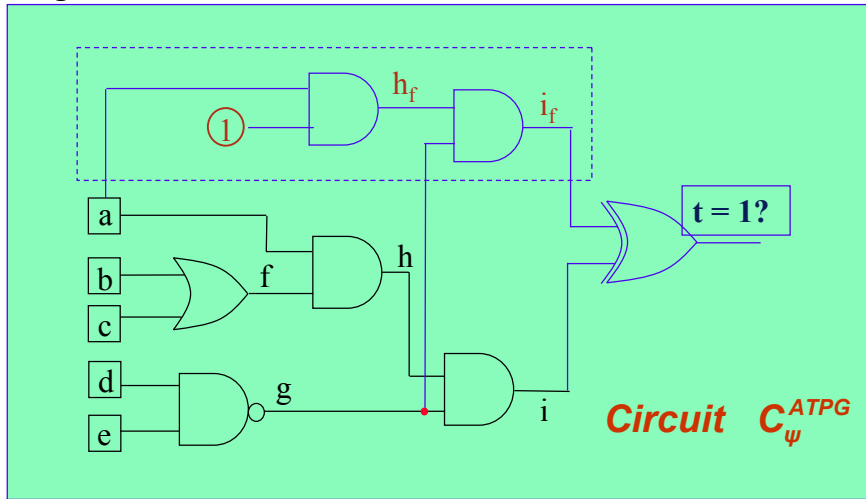
## ATPG as a CIRCUIT-SAT problem

Can we find an input value in which the faulty circuit and the good circuit differ?



43

## The Boolean Satisfiability (SAT) problem

Given a formula,  $f$  :

- ❖ Defined over a set of variables,  $V$  ( $a, b, c$ )
- ❖ Comprised of a conjunction of clauses ( $C_1, C_2, C_3$ )
- ❖ Each clause is a disjunction of literals of the variables  $V$

Does there exist an assignment of Boolean values to the variables,  $V$  which sets at least one literal in each clause to '1' ?

Example :  $(a + b + \bar{c})(\bar{a} + c)(a + \bar{b} + c)$        $a=b=c=1$


$\underbrace{\hspace{1.5cm}}_{C_1}$        $\underbrace{\hspace{1.5cm}}_{C_2}$        $\underbrace{\hspace{1.5cm}}_{C_3}$

44
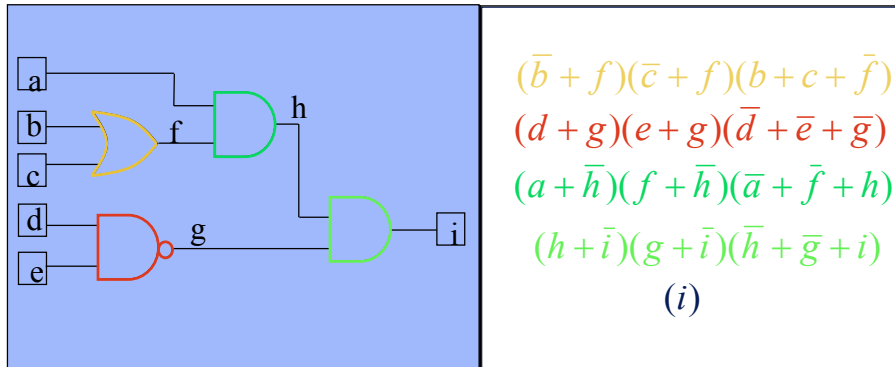
# CIRCUIT-SAT as a SAT problem

A set of clauses representing the functionality of each gate

A unit literal (*i*) clause asserting the output to be '1'



$$\begin{aligned}
 &(\bar{b} + f)(\bar{c} + f)(b + c + \bar{f}) \\
 &(d + g)(e + g)(\bar{d} + \bar{e} + \bar{g}) \\
 &(a + \bar{h})(f + \bar{h})(\bar{a} + \bar{f} + h) \\
 &(h + i)(g + i)(\bar{h} + \bar{g} + i) \\
 &(i)
 \end{aligned}$$

45


## Algorithm for SAT [DPLL-62]

*We have reduced ATPG to SAT- but then what?*

**Given :** CNF formula  $f(v_1, v_2, \dots, v_k)$ , and an ordering function *Next\_Variable*

```

 
Is_SAT(f, A)
{
  if Check_SAT(f, A) return SAT
  if Check_UNSAT(f, A) return UNSAT
  v = Next_Variable(f, A)
  if Is_SAT(f, (A, v=0)) return SAT
  if Is_SAT(f, (A, v=1)) return SAT
  return UNSAT
}
    
```



46
 
## DPLL Algorithm – Unit Clause Rule


- Unit Literal Propagation rule (Boolean Constraint Propagation, BCP)



47

## DPLL Algorithm – Pure Literal Rule

- Pure-Literal rule:  $a$

 


48



## Tegus Performance on Real Circuits
 
### Results :

- Of the 11,000 instances generated, 90% were solved in less than 1/100th of a second
- The remaining exhibited roughly a cubic growth in execution time



**Why is ATPG Easy (although NP-Complete)?**

49

## Current Status on Manufacture Test

Practical approach to test: use scan – achieve 99%+ stuck-at coverage

Single stuck-at-fault testing for combinational logic is a “solved problem”

- Despite the fact that it is NP-complete
- After 20+ years of research
- Results applied to combinational-equivalence checking

Single stuck-at-fault testing for sequential circuits is an intractable problem

- Despite the fact that it is also (only) NP-complete
- Even after 20+ years of research
- Time-frame expansion used in state-space search

Principal research focus is on ATPG for enhanced fault models

- Delay fault testing

Other approaches

- BIST

50

## PODEM

```
PODEM(po, lvalue) {  
  
    jlist = po with logical value lvalue;  
  
    status = SEARCH_1(jlist);  
    return(status);  
}
```

51

## SEARCH\_1(jlist)

```
SEARCH_1(jlist)  
{  
    if (length of jlist is zero) return SUCCEED;  
  
    if (BACKTRACE(po, po_value, &pi, &pi_value) == FALSE)  
        return(FAILED);  
    if (IMPLY(pi, pi_value, jlist) != IMPLY_CONFLICT) {  
        search_status = SEARCH_1(JLIST);  
        if (search_status == FAILED) {  
            restore the state of the network to what it was  
            prior to the most recent primary input assignment;  
            search_status = SEARCH_2(jlist, pi, 1 - pi_value);  
        }  
    } else {  
        restore the state of the network;  
        search_status = SEARCH_2(jlist, pi, 1 - pi value);  
    }  
    return(search_status);  
}
```

52

## SEARCH\_2(jlist)

```
SEARCH_2(jlist, pi, pi_value)
{
    backtracks = backtracks + 1;
    if (backtracks > BACKTRACK_LIMIT) return(ABORTED);
    if(IMPLY(pi, pi_value, jlist) != IMPLY_CONFLICT) {
        search_status = SEARCH_1(jlist);
        if (search_status == FAILED) {
            restore the state of the network;
        } else {
            search_status = FAILED;
            restore the state of the network;
        }
    }
    return(search_status);
}
```