

Technology Independent Multi-Level Logic Optimization

Prof. Kurt Keutzer


Prof. Sanjit Seshia

EECS



University of California, Berkeley, CA

Thanks to R. Rudell, S. Malik, R. Rutenbar



Logic Optimization

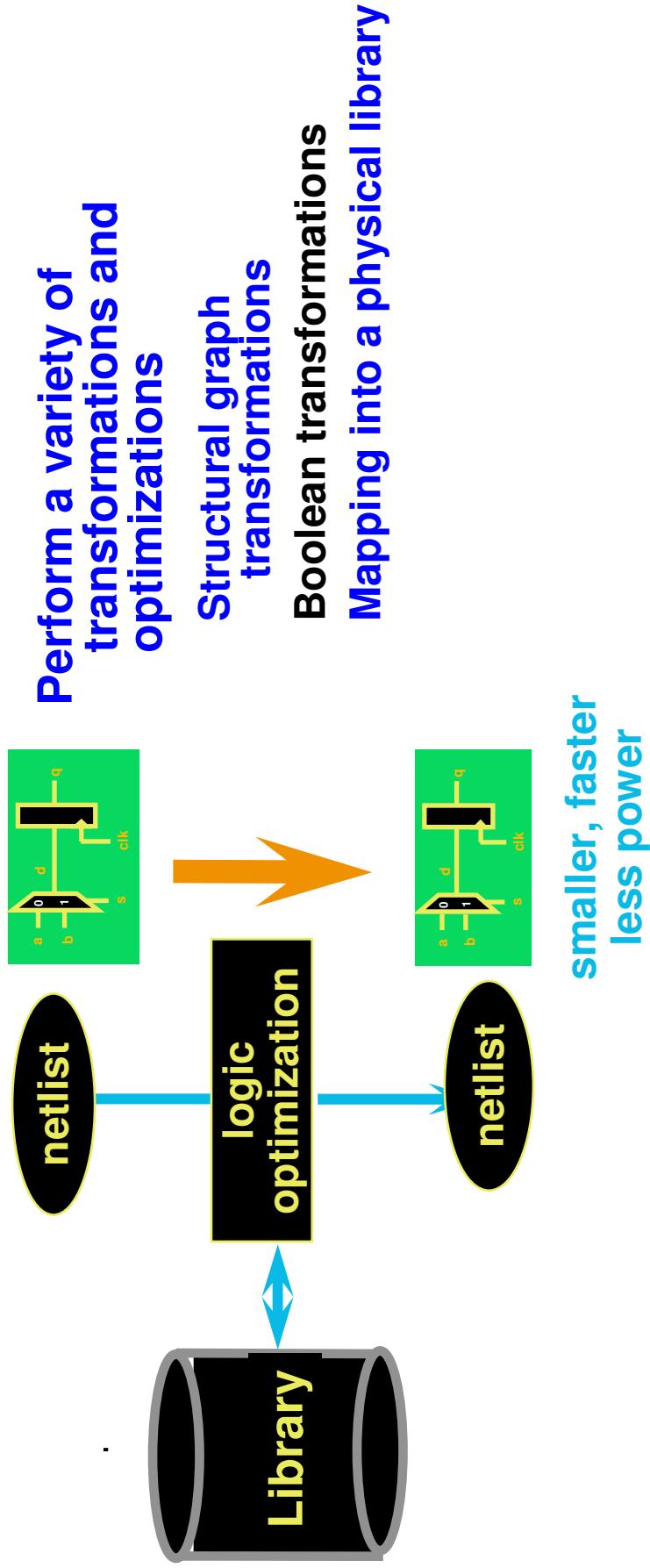

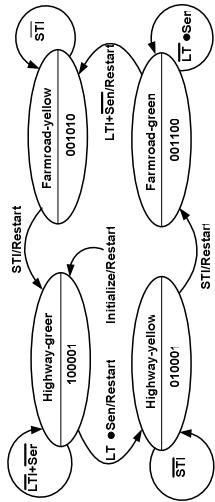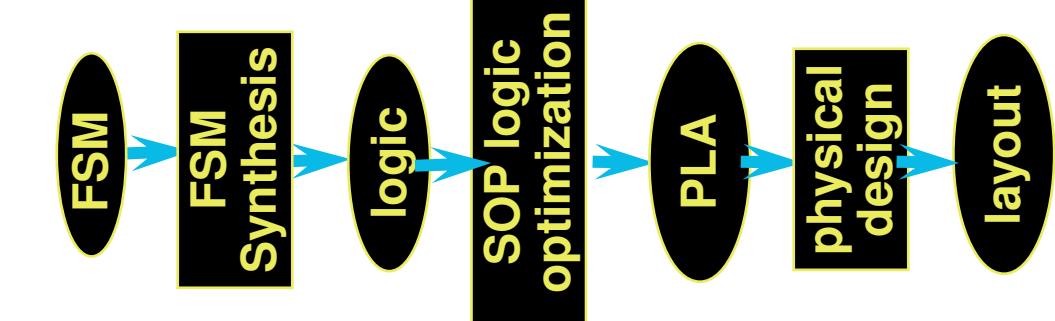
What We've Seen: Early “Synthesis” Flow & 2-Level Minimization



$$F1 = B + D + A C + A C$$

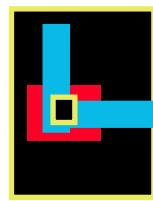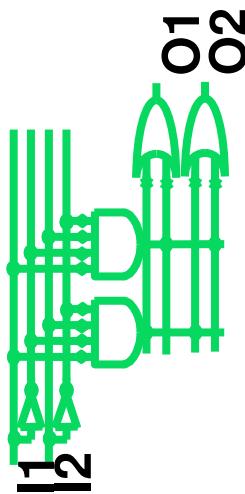

Reduce to Combinational Optimization

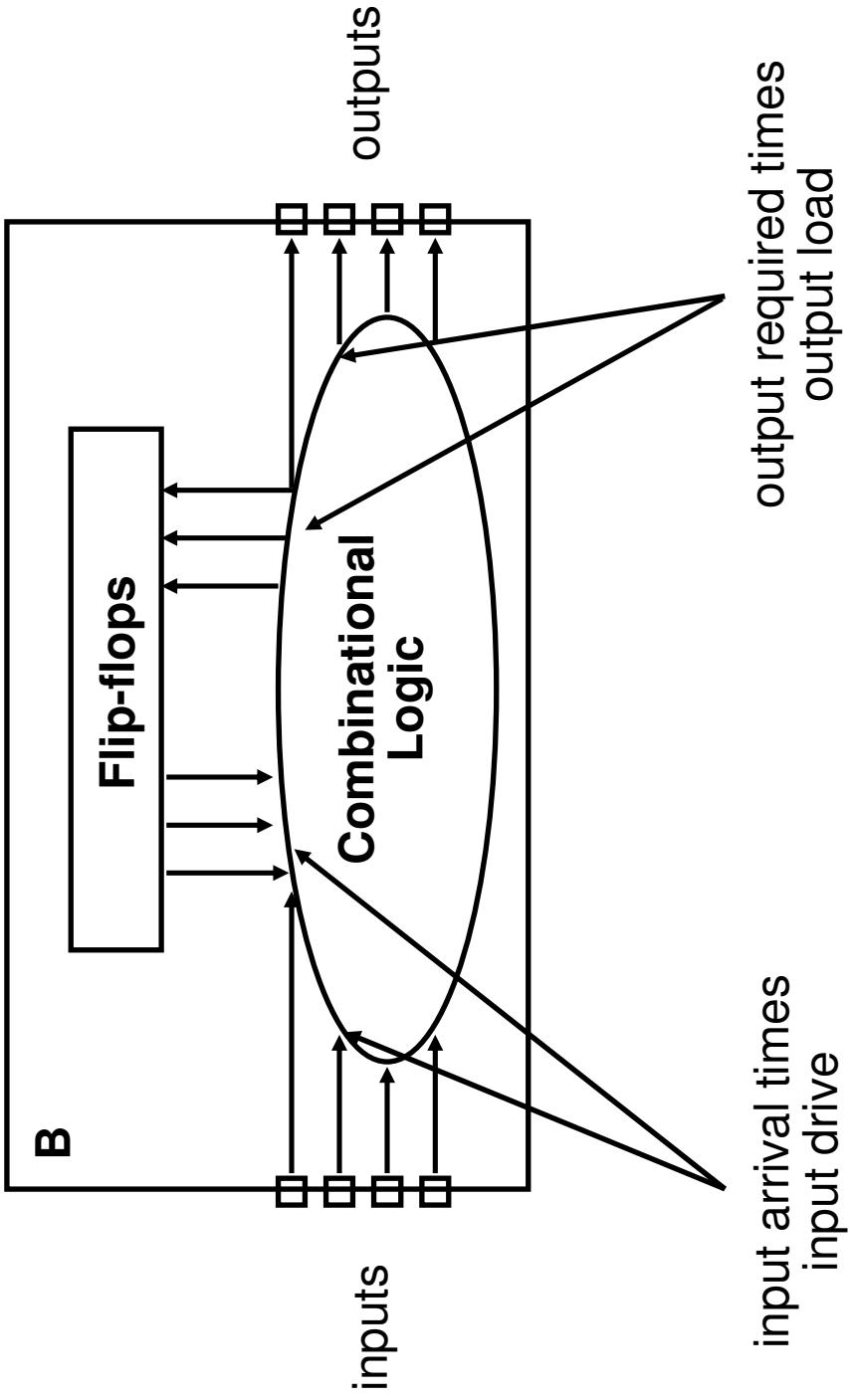

Combinational Logic Optimization

Input:

Initial Boolean circuit

Timing characterization for the module

- input arrival times and drive factors
- output loading factors

Optimization goals

- output required times output load

Target library description

Output:

Minimum-area net-list of library gates which meets timing constraints

A very difficult optimization problem !


Modern Approach to Logic Optimization

Divide logic optimization into two subproblems:

- Technology-independent optimization
 - determine overall logic structure
 - estimate costs (mostly) independent of technology
 - simplified cost modeling
- Technology-dependent optimization (technology mapping)
 - binding onto the gates in the library
 - detailed technology-specific cost model

Orchestration of various optimization/transformation techniques for each subproblem

Logic Optimization

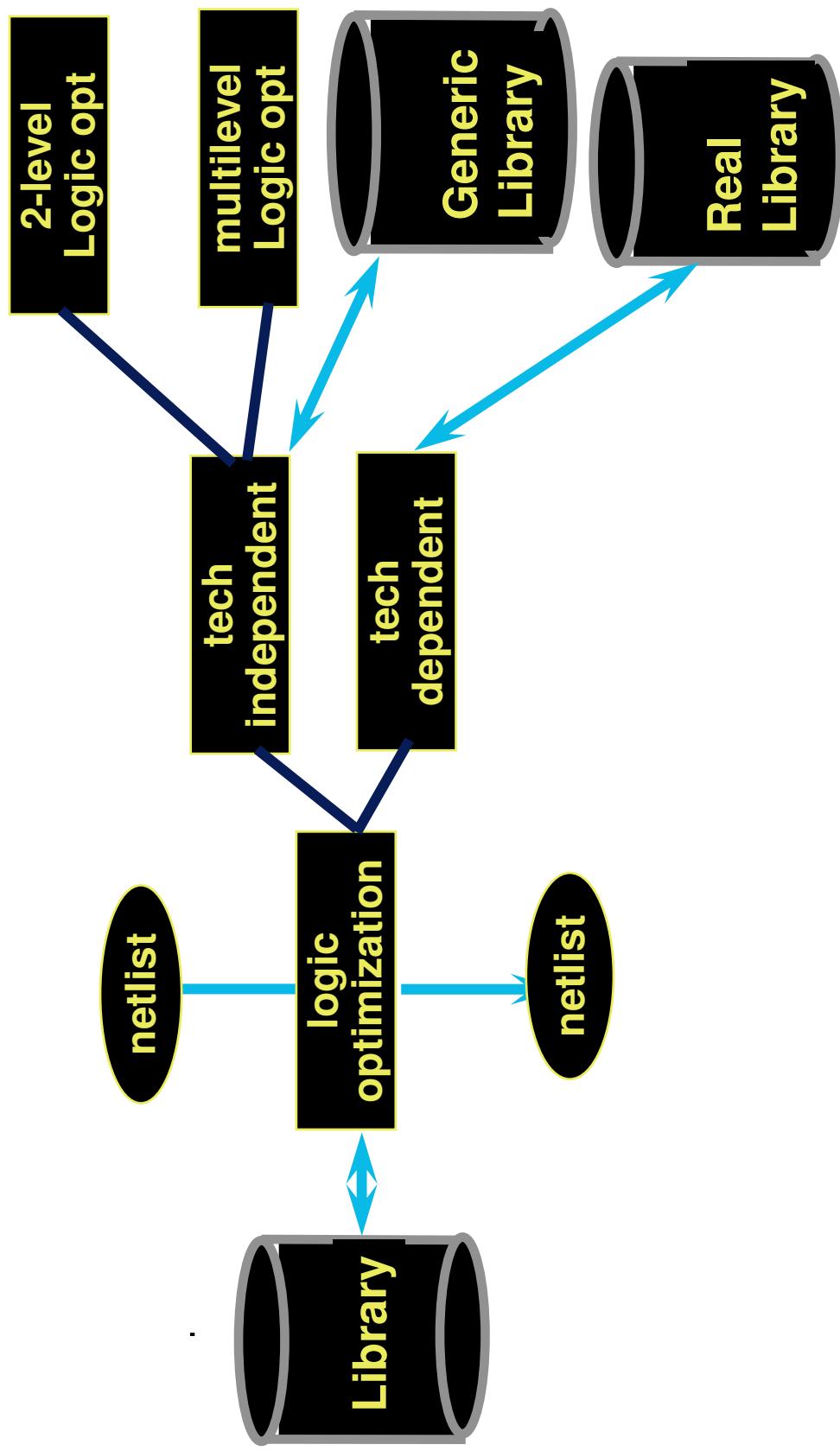

Outline

- Motivation for Multilevel Ckts
- Overview of Multilevel Optimization
- Details on Multilevel Optimization Techniques



Why Multilevel Combinational Circuits?

- There are many functions that are too “expensive” to implement in two-level form
 - Try 16-bit adder \Rightarrow 32 input lines and 2^{16} product terms!
- Delay vs. Area tradeoff
 - 2-level ckt: tiny delay, large area (many gates & literals)
 - multi-level: bigger delay, less area

Outline

- **Motivation for Multilevel Ckts**
- **Overview of Multilevel Optimization**
- **Details on Multilevel Optimization Techniques**

Representation: Boolean Network

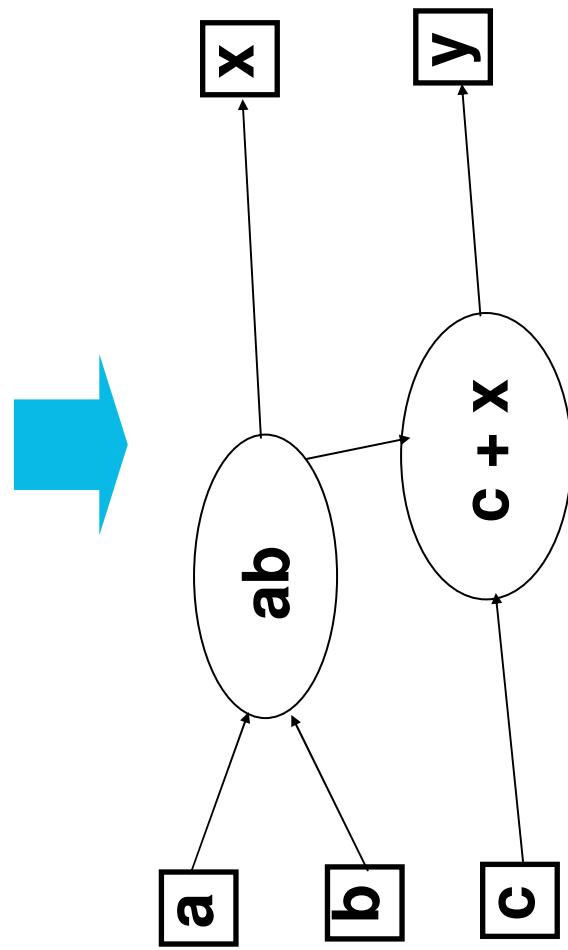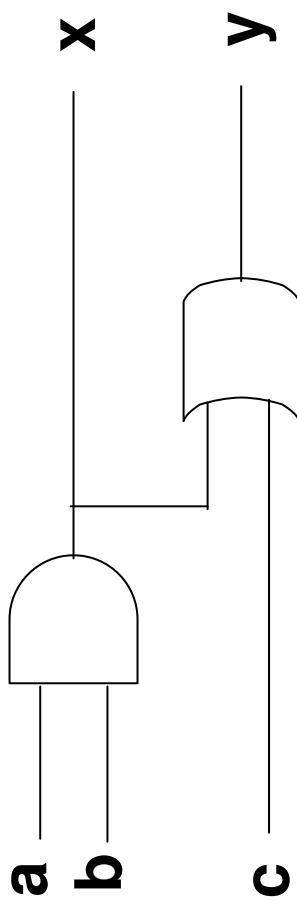

Boolean Network, Explained

- It's a graph:

- Primary inputs (variables)
- Primary outputs
- Intermediate nodes (in SOP form in terms of its inputs)

- Generic library – technology independent

- Has standard functions – ND2, ND4, AOI22

- Quality of network: area, delay, ...
 - measured in terms of #(literals), depth, ...

Tech.-Independent Multi-Level Optimization: Operations

Involves performing the following operations “iteratively” until “good enough” result is obtained:

1. Simplification
 - Minimizing two-level logic function (SOP for a single node)
2. Elimination
 - Substituting one expression into another.
3. Decomposition
 - Expressing a single SOP with 2 or more simpler forms
4. Extraction
 - Finding & pulling out subexpressions common to many nodes
5. Substitution
 - Like extraction, but nodes in the network are re-used

Example

(due to G. De Micheli)

a

$v = a'd + bd + c'd + ae'$

w

b

$p = ce + de$

c

$s = r + b'$

x

$t = ac + ad + bc + bd + e$

d

y

e

z

$u = q'c + qc' + qc$

#literals = 33, depth = 3

Example: Elimination

a

$$v = a'd + bd + c'd + ae'$$

w

b

$$p = ce + de$$

x

$$p = p + a'$$

$$s = r + b'$$

c

d

y

$$t = ac + ad + bc + bd + e$$

e

$$u = q'c + qc' + qc$$

z

#literals = 33, depth = 3

Example: Eliminate node r

a

$$v = a'd + bd + c'd + ae'$$

w

b

$$p = ce + de$$

x

c

$$s = p + a' + b'$$

y

d

$$t = ac + ad + bc + bd + e$$

z

e

$$q = a + b$$

$$u = q'c + qc' + qc$$

#literals = 32, depth = 2

Example: Simplification

a

$$v = a'd + bd + c'd + ae'$$

b

$$p = ce + de$$

c

$$s = p + a' + b'$$

d

$$t = ac + ad + bc + bd + e$$

e

$$u = q'c + qc' + qc$$

w

x

y

z

#literals = 32, depth = 2

Example: Simplifying node u

a

b

c

d

e

$$v = a'd + bd + c'd + ae'$$

$$p = ce + de$$

$$t = ac + ad + bc + bd + e$$

$$q = a + b$$

w

x

y

z

#literals = 28, depth = 2

Example: Decomposition

a

$v = a'd + bd + c'd + ae'$

w

b

$p = ce + de$

x

c

$s = p + a' + b'$

y

d

$t = ac + ad + bc + bd + e$

z

e

$u = q + c$

#literals = 28, depth = 2

Example: Decomposing node v

a

j = a' + b + c'

w

b

p = ce + de

x

c

s = p + a' + b'

y

d

t = ac + ad + bc + bd + e

z

e

u = q + c

#literals = 27, depth = 2

Example: Extraction

a

j = a' + b + c'

w

b

p = ce + de

x

c

s = p + a' + b'

y

d

t = ac + ad + bc + bd + e

z

e

q = a + b

u = q + c

#literals = 27, depth = 2

Example: Extracting from p and t

a

j = a' + b + c'

v = jd + ae'

w

b

p = ke

s = p + a' + b'

x

c

k = c + d

t = ka + kb + e

y

d

q = a + b

z

#literals = 23, depth = 3

Example: What next?

a

j = a' + b + c'

v = jd + ae'

w

b

p = ke

s = p + a' + b'

x

c

k = c + d

t = ka + kb + e

y

d

q = a + b

u = q + c

z

#literals = 23, depth = 3

Which Operations Do We Know How to Do?

Involves performing the following operations
“iteratively” until “good enough” result is obtained:

- 1. Simplification**
 - Minimizing two-level logic function (SOP for a single node)
- 2. Elimination**
 - Substituting one expression into another.
- 3. Decomposition**
 - Expressing a single SOP with 2 or more simpler forms
- 4. Extraction**
 - Finding & pulling out subexpressions common to many nodes
- 5. Substitution**
 - Like extraction, but nodes in the network are re-used

Outline

- Motivation for Multilevel Ckts
- Overview of Multilevel Optimization
- Details on Multilevel Optimization Techniques

Need for Factoring/Division

Factored versus Disjunctive forms

$$f = ac + ad + bc + bd + a\bar{e}$$

sum-of-products or disjunctive form

$$f = (a + b)(c + d) + a\bar{e}$$

factored form

multi-level or complex gate

What we need is a way to do “division”

Divisors and Decomposition

Given Boolean function F , we want to write it as

$$F = D \cdot Q + R$$

where D – Divisor, Q – Quotient, R – Remainder

Decomposition: Searching for divisors which are common to many functions in the network

- identify divisors which are common to several functions
- introduce common divisor as a new node
- re-express existing nodes using the new divisor

Boolean Division

Given Boolean function F , we want to write it as

$$F = D \cdot Q + R$$

- **D is a factor of F iff $F \cdot D' = 0$**
 - ON-SET(D) contains ON-SET(F)
- **If $F \cdot D \neq 0$, then D is a divisor of F**
- **How many possible factors D can there be for a given F?**

Algebraic Model

Idea: Perform division using only the rules (axioms) of real numbers, not all of Boolean algebra

Real Numbers

$$a \cdot b = b \cdot a$$

$$a + b = b + a$$

$$a \cdot (b \cdot c) = (a \cdot b) \cdot c$$

$$a + (b + c) = (a + b) + c$$

$$a \cdot (b + c) = a \cdot b + a \cdot c$$

$$a \cdot 1 = a \quad a \cdot 0 = 0 \quad a + 0 = a$$

Boolean Algebra

$$a \cdot b = b \cdot a$$

$$a + b = b + a$$

$$a \cdot (b \cdot c) = (a \cdot b) \cdot c$$

$$a + (b + c) = (a + b) + c$$

$$a \cdot (b + c) = a \cdot b + a \cdot c$$

$$a \cdot 1 = a \quad a \cdot 0 = 0 \quad a + 0 = a$$

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

$$a + a' = 1 \quad a \cdot a' = 0 \quad a \cdot a = a \quad a + a = a$$

$$a + 1 = 1 \quad a + ab = a \quad a \cdot (a + b) = a$$

...

Algebraic Division

- A literal and its complement are treated as unrelated
 - Each literal as a fresh variable
 - E.g.
$$f = ab + a'x + b'y \quad \text{as} \quad f = ab + dx + ey$$
- Treat SOP expression as a polynomial
 - Division/factoring then becomes polynomial division/factoring
- Boolean identities are ignored
 - Except in pre-processing
 - Simple local simplifications like $a + ab \rightarrow a$ performed

Algebraic vs. Boolean factorization

$$f = a\bar{b} + a\bar{c} + b\bar{a} + b\bar{c} + c\bar{a} + c\bar{b}$$

Algebraic factorization produces

$$f = a(\bar{b} + \bar{c}) + \bar{a}(b + c) + b\bar{c} + c\bar{b}$$

Boolean factorization produces

$$f = (a + b + c)(\bar{a} + \bar{b} + \bar{c})$$

Algebraic Division Example

$$F = ac + ad + bc + bd + e$$

Want to get Q, R, where $F = DQ + R$ for

1. $D = a + b$

2. $D = a$

Algebraic Division Algorithm

- What we want:
 - Given F, D , find Q, R
 - F, D expressed as sets of cubes (same for Q, R)
- Approach:
 - For each cube C in D {
 let $B = \{\text{cubes in } F \text{ contained in } C\}$
 if (B is empty) **return** $Q = \{\}, R = F$
 let $B = \{\text{cubes in } B \text{ with variables in } C \text{ removed}\}$
 if (C is the first cube in D we're looking at)
 let $Q = B;$
 else $Q = Q \cap B;$
 }
 }
 R = $F \setminus (Q \times D);$
 Complexity?

Taking Stock

- **What we know:**
 - How to perform Algebraic division given a divisor D
- **What we don't**
 - How to pick D?
- **Recall what we wanted to do:**
 - Given 2 functions F and G, find a common divisor D and factorize them as
 - $F = D Q_1 + R_1$
 - $G = D Q_2 + R_2$

New Terminology: Kernels

- A kernel of a Boolean expression F is a **cube-free expression** that results when you divide F by a single cube
 - That “single cube” is called a co-kernel
- Cube-free expression: Cannot factor out a single cube that leaves behind no remainder
- Examples: Which are cube-free?
 - $F = a$
 - $F = a + b$
 - $F = abc + abd$

Kernels: Examples

$$F = ae + be + cde + ab$$

$K(f)$	Kernel	Co-kernel
$\{a,b,cd\}$	e	$?$
$\{e,b\}$	$?$	b
$?$		
$\{ae,be,cde,ab\}$		$?$

Why are Kernels Useful?

Goal of multi-level logic optimizer is to find common divisors of two (or more) functions f and g

Theorem: [Brayton & McMullen]

f and g have a non-trivial (multiple-cube) common divisor d if and only if there exist kernels $k_f \in K(f)$, $k_g \in K(g)$ such that $k_f \cap k_g$ is non-trivial, i.e., not a cube

∴ can use kernels of f and g to locate common divisors

Theorem, Put Another Way

- $F = D1 \cdot K1 + R1$
- $G = D2 \cdot K2 + R2$
- $K1 = (X + Y + \dots) + \text{stuff1}$
- $K2 = (X + Y + \dots) + \text{stuff2}$
- Then,
 - $F = (X + Y + \dots) D1 + \text{stuff3}$
 - $G = (X + Y + \dots) D2 + \text{stuff4}$
- So, if we find kernels and intersect them, the intersection gives us our common divisor

Kernel Intersection: Example

$$F = ae + be + cde + ab$$

$$G = ad + ae + bd + be + bc$$


$K(f)$	$K(g)$	Kernel	Co-kernel	Co-kernel
$\{a,b,cd\}$	e	$\{a,b\}$	d or e	
$\{e,b\}$	a	$\{d,e\}$	a or b	
$\{e,a\}$	b	$\{d,e,c\}$	b	
$\{ae,be,cde,ab\}$	1	$\{ad,ae,bd,be,bc\}$	1	

How do we find Kernels?

Overview: Given a function F

1. Pick a variable x appearing in F , and use it as a divisor
2. Find the corresponding kernel K if one exists (at least 2 cubes in F contain x)
 - If not, go back to (1) and pick another variable
3. Use K in place of F and recurse to find kernels of K
 - $F = x K + R$ and $K = y M + S \rightarrow F = xy M + \dots$
 - Add kernels of K to those of F
4. Go back to (1) and pick another variable to keep finding kernels

Finding Kernels: Example

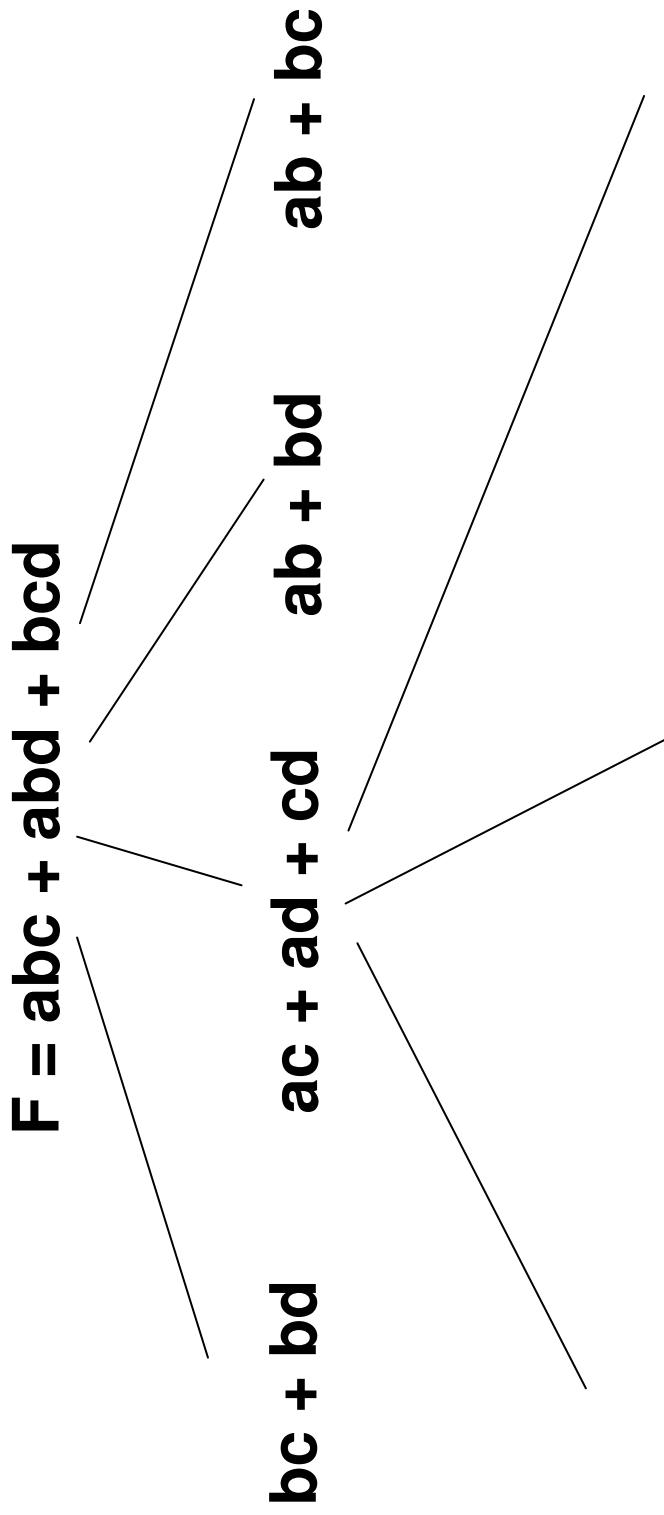

Can we do better?

Finding Kernels: Example

$F = abc + abd + bcd$

$bc + bd$ $abc + ad + cd$ $abc \& bcd$ $ab + bc$

both contain c.

Intersection is bc.

Recurse on $F/bc = a+d$

Take intersection of all cubes containing a variable

Kernel Finding Algorithm

```
FindKernels(F) {  
    K = {};  
    for (each variable x in F) {  
        if (F has at least 2 cubes containing x) {  
            let S = {cubes in f containing x};  
            let c = cube resulting from intersection of all cubes in S  
            K = K ∪ FindKernels(F/c); //recursion  
        }  
    }  
    K = K ∪ F;  
    return K;  
}
```

Strong (or Boolean) Division

Given a function f to be strong divided by g

Add an extra input to f corresponding to g ,
namely G and obtain function h as follows

$$h_{DC} = G\bar{g} + \bar{G}g \quad \xrightarrow{\text{Inputs to } f \text{ that}} \quad \text{cannot occur}$$
$$h_{ON} = f_{ON} - h_{DC}$$
$$h_{OFF} = \frac{f_{ON} + h_{DC}}{f_{ON} + h_{DC}}$$

Minimize h using two-level minimizer

$$\text{Get: } h = QG + R$$

Additional Reading

1. Read Chapter 7 upto Sec. 7.6

2. R. Rudell, ‘Logic Synthesis for VLSI Design’,
PhD Thesis, UC Berkeley, 1989.

3. R. Brayton, G. Hachtel, A. Sangiovanni-Vincentelli, ‘Multilevel Logic Synthesis’,
Proceedings of the IEEE, Feb’90.

OPTIONAL

Logic optimization - summary

Current formulation of logic synthesis and optimization is the most common techniques for designing integrated circuits today

Has been the most successful design paradigm 1989 - present

Almost all digital circuits are touched by logic synthesis

- **Microprocessors (control portions/random glue logic ~ 20%)**
- **Application specific standard parts (ASSPs)- 20 - 90%**
- **Application specific integrated circuits (ASICs) - 40 - 100%**

Real logic optimization systems orchestrate optimizations

- **Technology independent**
- **Technology dependent ← NEXT LECTURE**
- **Application specific (e.g. datapath oriented)**